
 



Verification of Inputs for Half Adder

 



Verification of Inputs for Half Subtractor




Verification of Inputs for Full Adder

 


 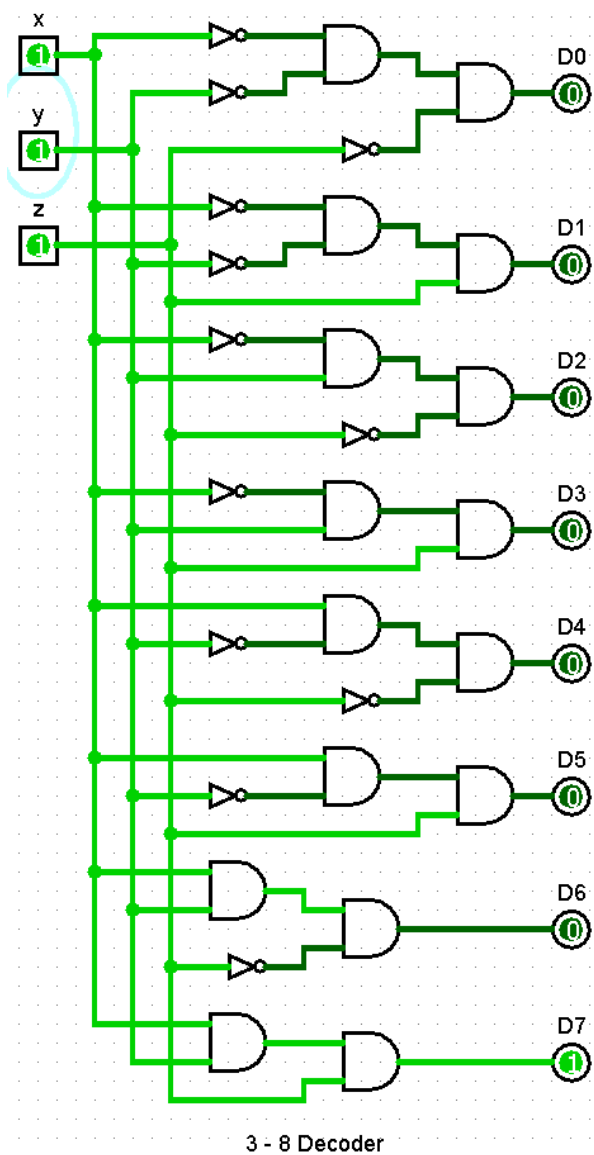Verification of Inputs for Full Subtractor




 

4-1 Mux

 

1-4 Demux

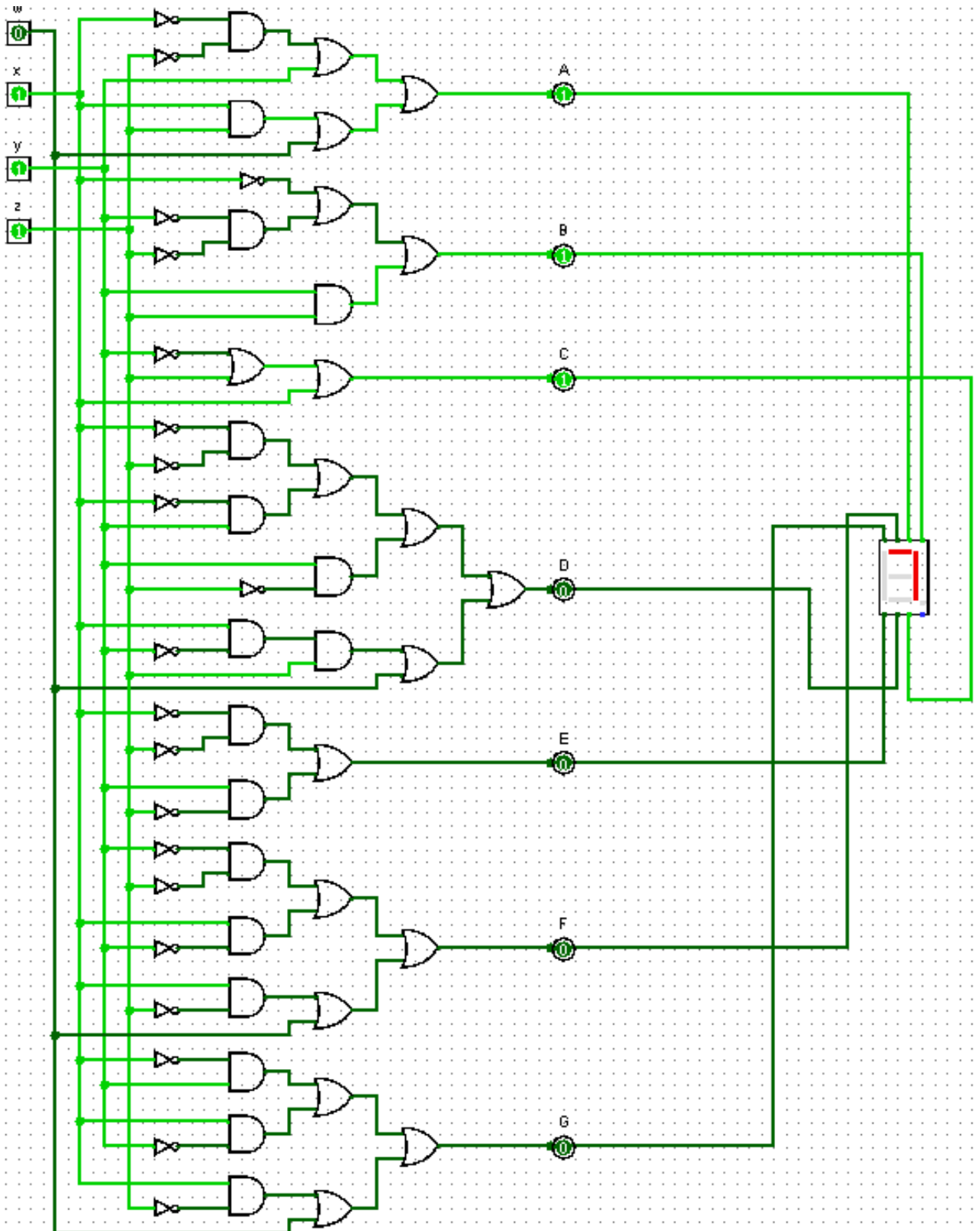

7 Segment Display

